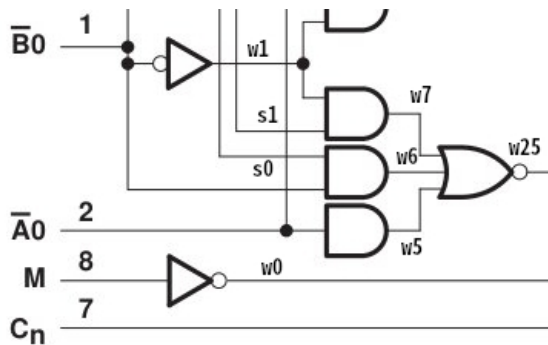


Lab: Specification of Texas Instrument sn74181 ALU

See the background information for the human readable specification of the TI sn74181. The ALU takes two 4-bit inputs, $\overline{A0}, \overline{A1}, \overline{A2}, \overline{A3}, \overline{B0}, \overline{B1}, \overline{B2}, \overline{B3}$ plus a carry bit C_n , and five selector bits, $S0, S1, S2, S3$ and M . Depending on the selector bit values, various operations can be performed on the input bits with results appearing on output bits $\overline{G}, C_{n+4}, \overline{P}, A=B, \overline{F0}, \overline{F1}, \overline{F2}, \overline{F3}$. In the following the overbars will not be displayed for simplicity and clarity. In the following a functional specification and a wiring specification for the ALU will be developed and the two will be shown equivalent.

Exercise 1:

Write the specification for the wiring diagram. The following will be a helpful beginning. Consider the following piece of the wiring diagram taken from Page 4 of the TI spec sheet:



Labels have been given to the interconnect points. These labels represent new variables that have logic values as indicated in the wiring specification. For example, w_0 has value $\sim M$ (use \sim for logical not), variable w_1 has value $\sim B_0$, variable w_5 has value A_0 (we remove overbars), variable w_6 has value $s_0 \wedge B_0$, w_7 has value $s_1 \wedge w_1$ and w_{25} has value $\sim(w_5 \vee w_6 \vee w_7)$. So, the description of the wiring can begin as a function like this:

```
f74181_netlist c a0 a1 a2 a3 b0 b1 b2 b3 m s0 s1 s2 s3 = [f0,f1,f2,f3,cout,p,g,a_b]
where
  w0 = ~m
  w1 = ~b0
  w5 = a0
  w6 = s0 /\ b0
  w7 = s1 /\ w1
  w25 = ~(w5 \/ w6 \/ w7)
```

All ALU inputs are the arguments of the function `f74181_netlist`. The output will be a list of ALU outputs in an order that will match the output of a corresponding functional specification. In Cryptol = cannot be a part of a variable label so $a=b$ is represent here as `a_b`. Similarly, `cout` is used to represent C_{n+4} . All overbars are removed and lower case letters for variables are used for simplicity and clarity.

Exercise 2:

The riddle of the Bitcoin and the Tigers. There are nine rooms, each with a sign on its door. A Bitcoin is in one room and one room only. Other rooms may be empty or have tigers. A prisoner has been tasked to open the door to the room containing the Bitcoin. If that happens the prisoner takes the Bitcoin and is released from prison. If a door containing a Tiger is opened, the prisoner is eaten. If a door to an empty room is opened the prisoner is not eaten but remains in prison. The signs are:

ROOM 1: THE BITCOIN IS IN A ROOM WITH AN UNEVEN NUMBER

ROOM 2: THIS ROOM IS EMPTY

ROOM 3: EITHER SIGN 5 TELLS THE TRUTH, OR SIGN 7 IS LYING

ROOM 4: SIGN 1 IS LYING

ROOM 5: SIGN 2 IS LYING OR SIGN 4 TELLS THE TRUTH

ROOM 6: SIGN 3 IS LYING

ROOM 7: THE BITCOIN IS NOT IN ROOM 1

ROOM 8: THIS ROOM HOSTS A TIGER, AND ROOM 9 IS EMPTY

ROOM 9: THIS ROOM HOSTS A TIGER, AND SIGN 6 IS LYING

A sign on the door to a room containing the BITCOIN is True

A sign on the door to a room containing a TIGER is False

A sign on the door to an empty room could be True or False

If you know whether room 8 is empty, you uniquely know what room the Bitcoin is in

Write a function that enables finding the Bitcoin.

Note: If your function is called `FindBitcoin` then `:prove FindBitcoin` will confirm that the Bitcoin is found